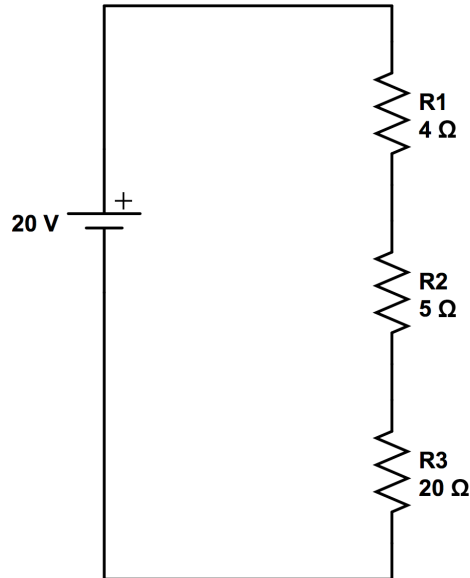


Quantitative Problems
(Given, Find, Solution REQUIRED)

1. Consider a three-bulb series circuit below.



Calculate the following:


- a. The current in R1.
- b. The current in R2.
- c. The current in R3.

- d. The voltage across R1.
- e. The voltage across R2.
- f. The voltage across R3.

- g. The power consumption of R1.
- h. The power consumption of R2.
- i. The power consumption of R3.
- j. The power supplied by the 20 V battery.

- k. The energy consumption of the circuit if left on for 24 hours a day for 31 days in [J],
- l. The energy consumption of the circuit if left on for 24 hours a day for 31 days in [kWh],
- m. The cost of operating the entire circuit for 24 hours a day for 31 days. The price of electricity is \$0.15/kWh.

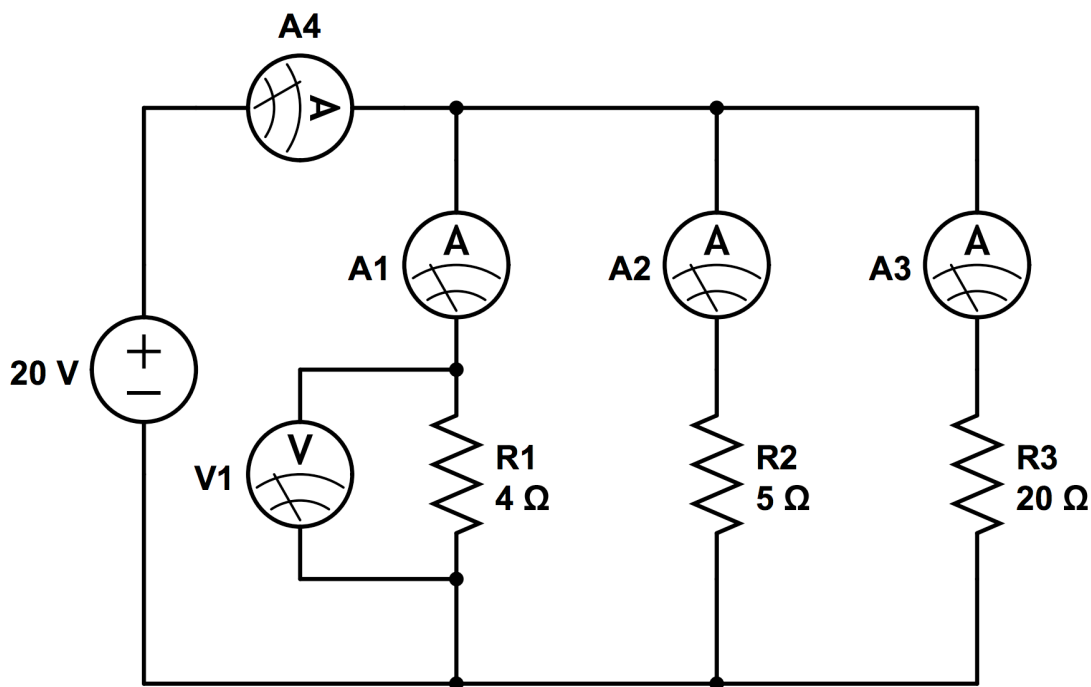
2. Consider the three-bulb parallel circuit below. Calculate the following:
- The current reading in A1.
 - The current reading in A2.
 - The current reading in A3.
 - The voltage across R1.
 - The voltage across R2.
 - The voltage across R3.
 - The power consumption of the bulb 1.
 - The power consumption of the bulb 2.
 - The power consumption of the bulb 3.
 - The power supplied by the 20 V battery.
 - The energy consumption of the entire circuit on for 24 hours a day for 31 days in [J].
 - The energy consumption of the entire circuit on for 24 hours a day for 31 days in [kWh].
 - The cost of operating the entire circuit for 24 hours a day for 31 days. The price of electricity is \$0.15/kWh.



Qualitative Problems


Short answer (in a complete sentence) or a fully labeled graph
(Given, Find, Solution NOT required)

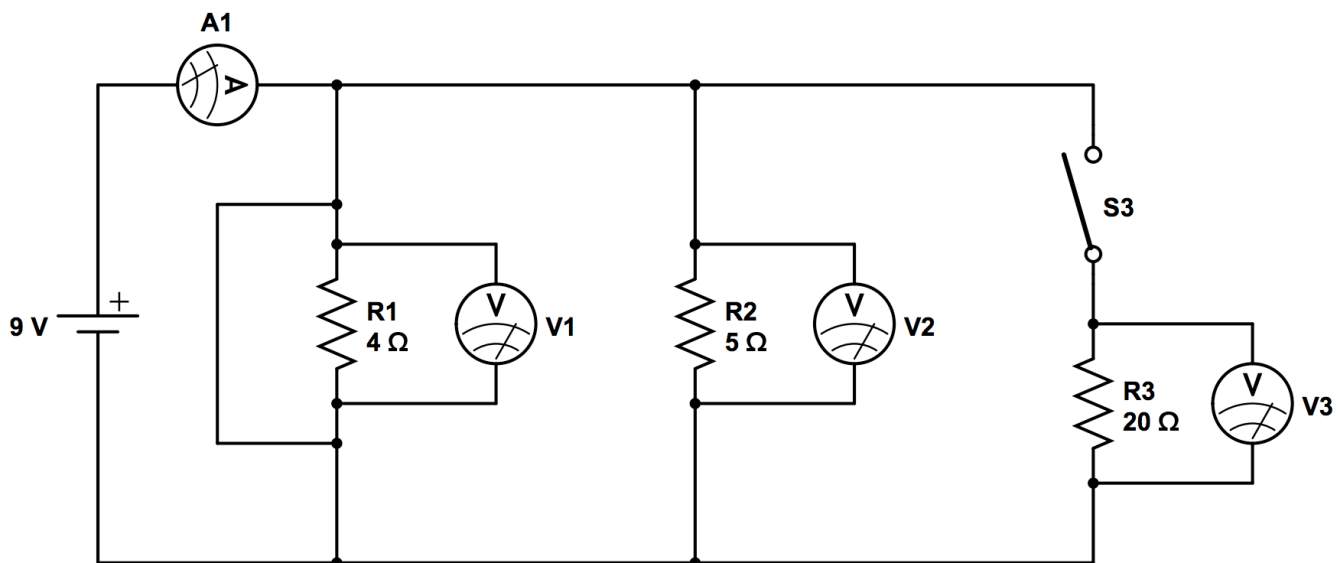3. Consider the three-bulb parallel circuit below. Answer each of the following questions and give a brief justification for your answer.
- What is the reading in voltmeter V1?
 - What is the reading in voltmeter V2?
 - What is the reading in voltmeter V3?
 - What is the reading in ammeter A1 if the resistance of the short circuit wire across R1 is $1\ \Omega$?



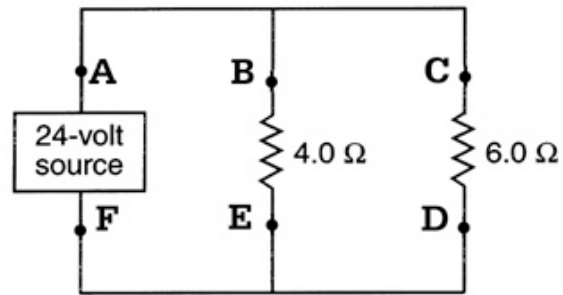4. Draw a series circuit with three bulbs, labeled bulb 1, bulb 2, and bulb 3, INCLUDING a switch that can turn bulb 2 “on” and “off”. What happens to the light intensity of bulbs 1 and 3 when bulb 2 is turned off?
5. Draw a parallel circuit with three bulbs, labeled bulb 1, bulb 2, and bulb 3, INCLUDING a switch that can turn bulb 2 “on” and “off”. What happens to the light intensity of bulbs 1 and 3 when bulb 2 is turned off?

Consider the following circuit for questions 6-8 below.



6. At what location(s) could a switch be placed in order to turn off both light bulbs?
7. At what location(s) could a switch be placed in order to turn off the 4Ω light bulb?
8. At what location(s) could a switch be placed in order to turn off the 6Ω light bulb?

HW Set 4 Answers

1a. 0.689 [A]
1b. 0.689 [A]
1c. 0.689 [A]

1d. 2.76 [V]
1e. 3.45 [V]
1f. 13.78 [V]

1g. 1.90 [W]
1h. 2.38 [W]
1i. 9.49 [W]
1j. 13.77 [W]

1k. 3.68×10^7 [J]
1l. 10.26 [kWh]
1m. \$ 1.53

2a. 5 [A]
2b. 4 [A]
2c. 1 [A]

2d. 20 [V]
2e. 20 [V]
2f. 20 [V]

2g. 100 [W]
2h. 80 [W]
2i. 20 [W]
2j. 200 [W]

2k. 5.36×10^8 [J]
2l. 148.8 [kWh]
2m. \$ 22.32

3-8. Will discuss in class